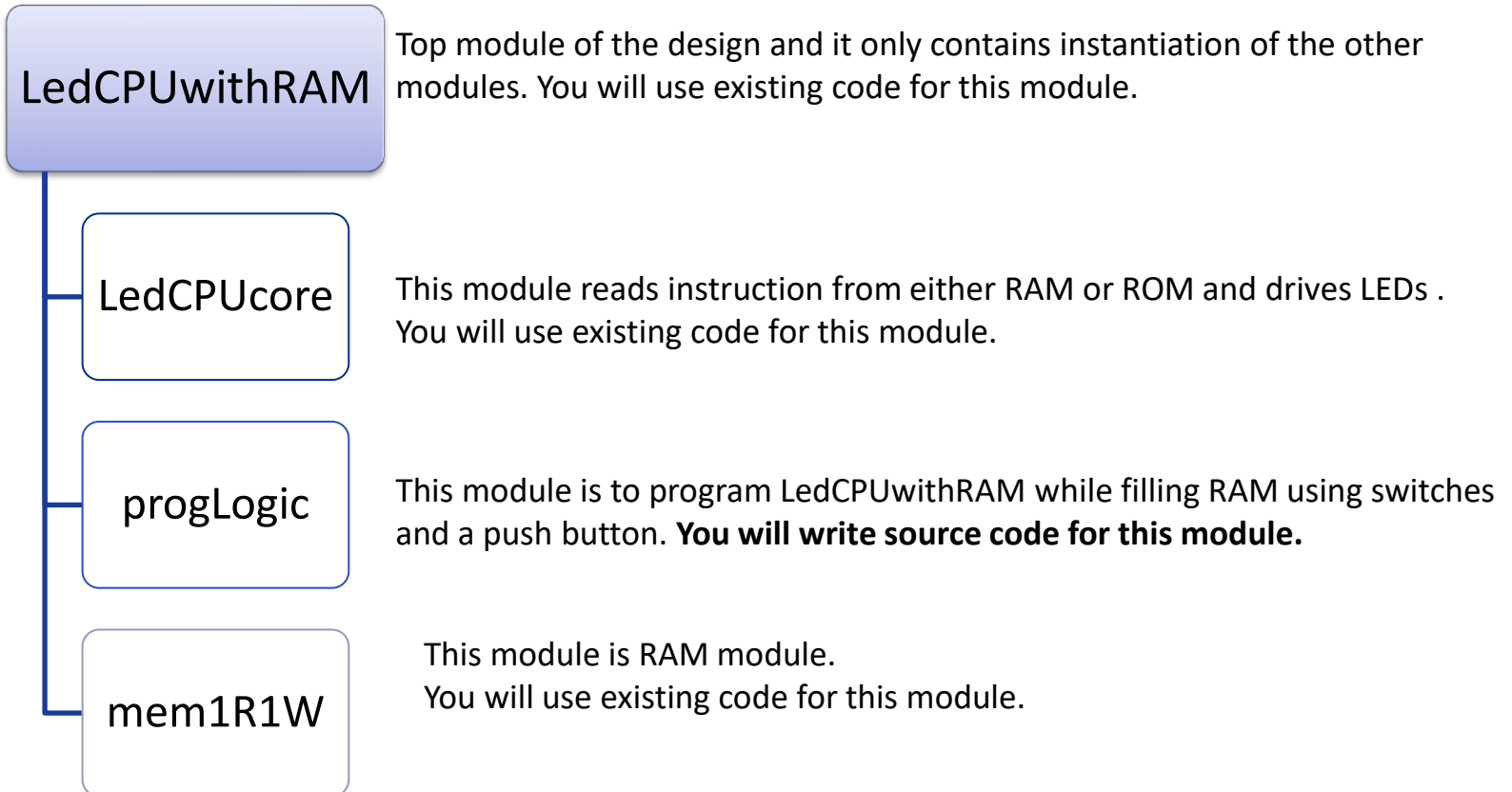


Led CPU With RAM


Design Description:

- It reads instructions from RAM instead of ROM, and executes these instructions.
- The difference between ROM and RAM CPU is that RAM CPU is programmable.
- It should execute 2 different commands like ROM CPU. These are jump and delay.

Hierarchy of LedCPUwithRAM




Block Diagram of LedCPUwithRAM

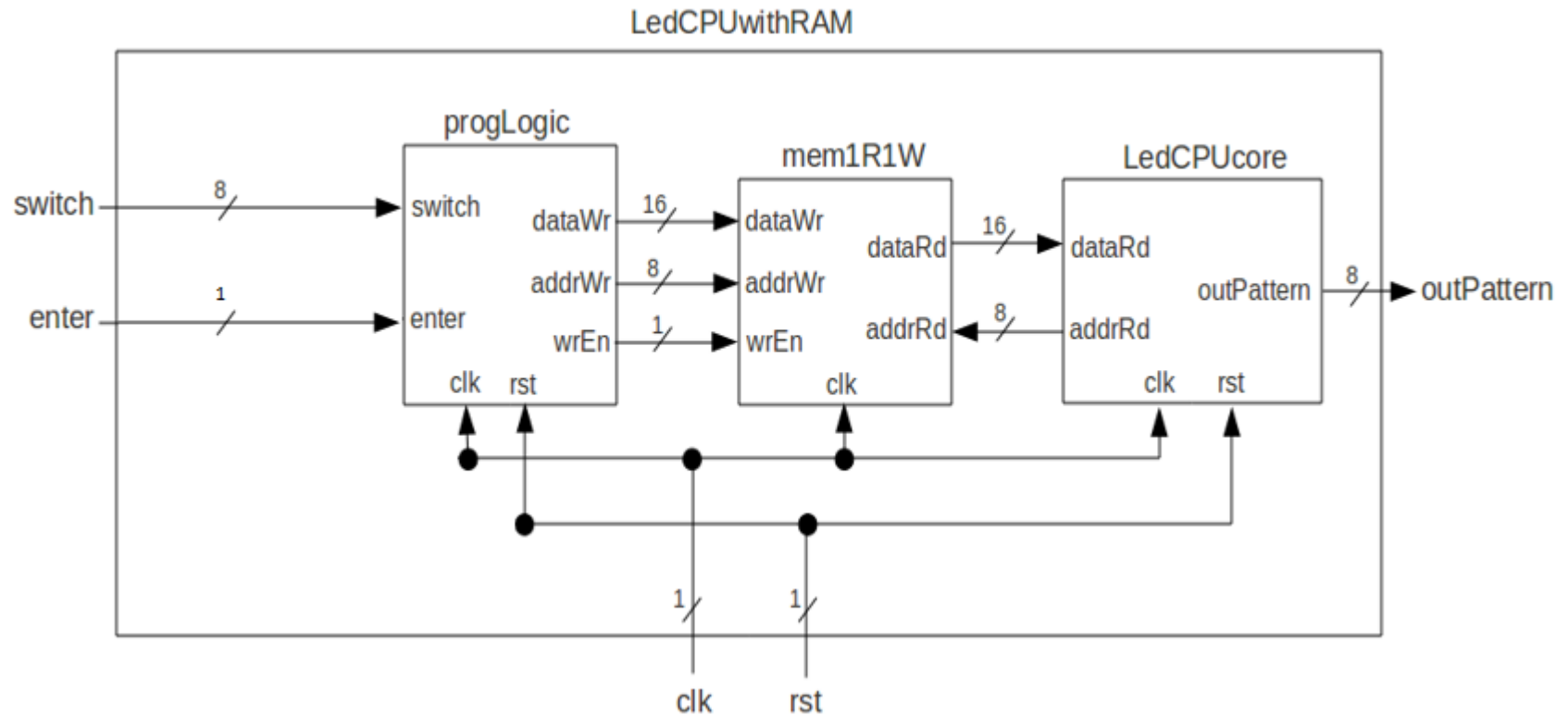

Design I/O:

clk	: 1 bit input for clock
rst	: 1 bit input for reset
switch	: 8 bits input comes from switches as data in
enter	: 1 bit input comes from a push button when data is ready on switches
dataWr	: 16 bits data output to RAM
addrWr	: 8 bits address output to RAM
wrEn	: 1 bits output as write enable to RAM

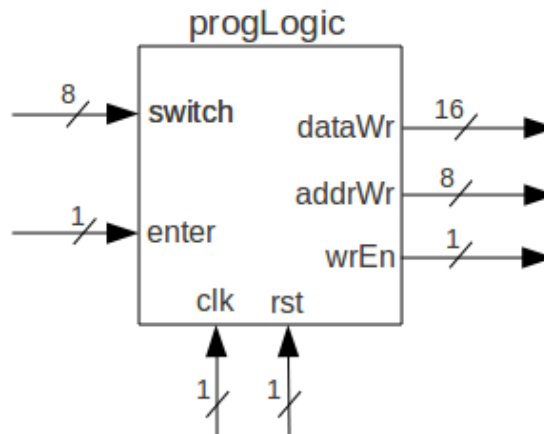

Design Behavior:

- The aim of this module is to fill RAM. RAM entries have 16 bits of length, and we will use 8 bits switches to fill it. So, we should first take 8 bits and then second 8 bits from switches.
- We will use an enter signal, which comes from a push button, as data ready signal.
- When the enter signal goes from 0 to 1 for first time, the data on switches will be our first 8 bits part of the 16 bits data. When for the second time the enter signal goes from 0 to 1, the data on switches will be our second 8 bits part of the 16 bits data.
- When 16 bits of data is ready, we should send this data to RAM while setting address location. Initial address location is 0 and it should increment 1 after 16 bits data was sent to RAM.
- Meanwhile wrEn signal should be 1 when we want to write data to RAM. Otherwise it should be 0.